

# Application of the UKRAA Very Low Frequency Receiver System

Whitham D. Reeve  
Anchorage, Alaska USA



Originally presented at

Society of Amateur Radio Astronomers  
2010 SARA Western Conference  
Mountain View, California  
March 20-21, 2010



## Contents

- Introduction
- Receiver system characteristics
- Kit construction
- Performance
- Conclusions



# INTRODUCTION



© 2010, 2026 Whitham D. Reeve

3

## Introduction

- The Very Low Frequency (VLF) receiver system is a useful sensor for monitoring Sudden Ionospheric Disturbances (SID) caused by solar flares
- A VLF receiver does not receive solar radio emissions directly
  - It receives terrestrial transmissions that propagate in the Earth-ionosphere waveguide
  - Solar flares change the waveguide's propagation characteristics and are indirectly observable with the receiver

© 2010, 2026 Whitham D. Reeve

4

## VLF Receivers

- A number of inexpensive amateur-designed VLF receivers have appeared over the years, for example
  - A Modular Receiver for Exploring the LF/VLF Bands, Coyle, L., QST, Part 1: Nov 2008, Part 2: Dec 2008
  - A Gyrator Tuned VLF Receiver, Communications Quarterly, Stokes, A., Spring 1994
  - Gyrator II - An Improved Gyrator Tuned VLF Receiver, Stokes, A., American Association of Variable Star Observers - Solar Division, Vol. 10, No. 1, Jul 1999
  - AMRAD Low Frequency Upconverter, Gentges, F & Ratzlaff, S., QST, Apr 2002

## VLF Receivers

- At least two receivers were professionally designed for educational purposes, for example
  - SolarSID and SuperSID, Stanford Solar Center, SID Monitors at: <http://solar-center.stanford.edu/SID/>
  - SuperSID available from Society of Amateur Radio Astronomers (SARA): <https://www.radio-astronomy.org/node/276>
- **Wideband (192 kHz & 96 kHz sample rate) soundcards also have been used**
  - **Not designed for connection to outdoor antenna without lightning protection**

## VLF Receivers

- Many receiver designs did not use a systems approach and some suffered serious limitations
- Many of the designs focused only on the receiver with little attention to the other parts of the receiving system
- A few were available as kits or already built
- **Software Defined Radio (SDR) Receivers now are a viable alternative**
  - **Notably: SDRPlay RSPxxx-series SDR Receivers**
  - **Other SDR Receivers with frequency range extending down to 10 kHz**

© 2010, 2026 Whitham D. Reeve

7

## UK Radio Astronomy Association

- In contrast, the UK Radio Astronomy Association (UKRAA) receiver is part of a modular system
  - Receiver
  - Loop antenna
  - Antenna tuning unit (ATU)
  - Optional signal generator for test and alignment
- Available as kit or already built

© 2010, 2026 Whitham D. Reeve

8

# UK Radio Astronomy Association




Loop  
Antenna



Receiver

Antenna Tuning Unit


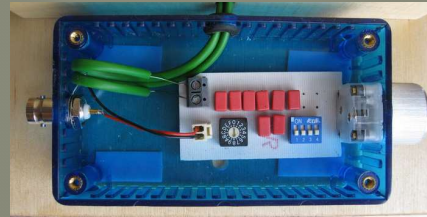


© 2010, 2026 Whitham D. Reeve

9
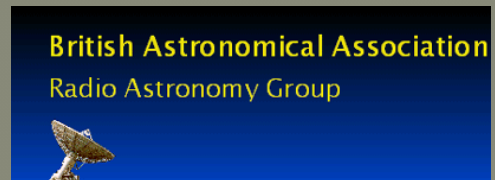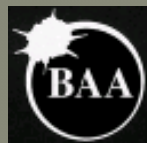
## UKRAA

- UK Radio Astronomy Association
  - [www.ukraa.com](http://www.ukraa.com)
  - Commercial arm of the British Astronomy Association (BAA) Radio Astronomy Group (RAG)
- BAA is the parent body of additional astronomy groups
  - [www.britastro.org](http://www.britastro.org)



© 2010, 2026 Whitham D. Reeve

10

## Prices (shipping extra) → 2010 : 2026 !


Description	Price (GBP)	Price (US\$)
VLF receiver kit, no enclosure	60.00 (67.00)	~96.00
VLF receiver assembled, no enclosure	90.00 (98.00)	~143.00
VLF receiver, assembled with enclosure	120.00 (130.00)	~191.00
Loop antenna kit, no wire	15.00 (26.00)	~24.00
Loop antenna kit, with wire	31.00 (50.00)	~49.00
Loop antenna, assembled	35.00 (N/A)	~56.00
Antenna tuning unit, assembled	25.00 (43.00)	~40.00
VLF signal generator	15.00 (25.00)	~24.00

Conversion factor was ~1.59 and presently ~1.36

## RECEIVER SYSTEM CHARACTERISTICS



## Receiver System Characteristics

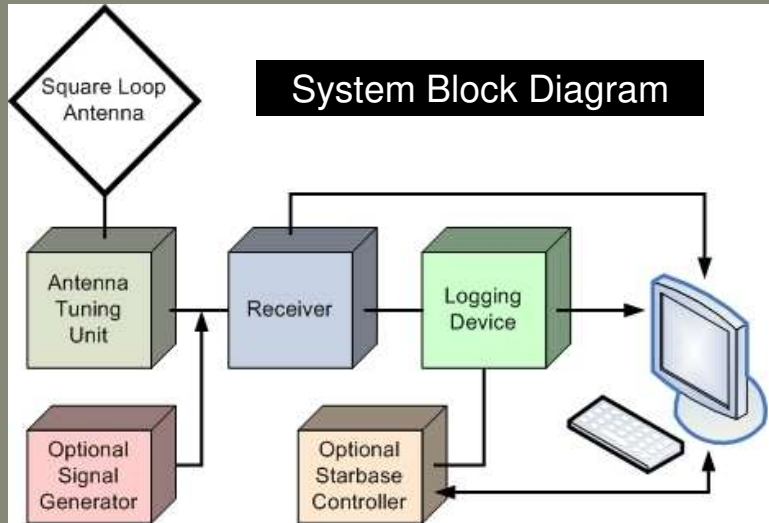

© 2010, 2026 Whitham D. Reeve

13

## Receiver System Characteristics

- Overall system design based on considerable experimentation by various UKRAA members
- Incorporates published and unpublished circuits by others




© 2010, 2026 Whitham D. Reeve

14
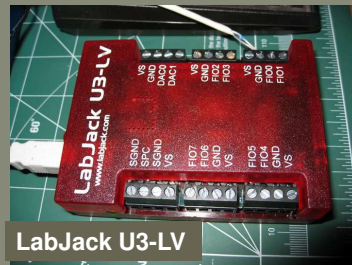
## Receiver System Characteristics

- Data output
  - Internal or external dc voltmeter for real-time display
  - External datalogger for charting and data archiving



© 2010, 2026 Whitham D. Reeve

15

## Optional Components

- Starbase controller  
(No Longer Available ?)
  - UKRAA hardware development project
  - Works with the Starbase software system
  - Can be used with a number of controllers and associated sensors, including VLF receivers and geomagnetometers




© 2010, 2026 Whitham D. Reeve

16
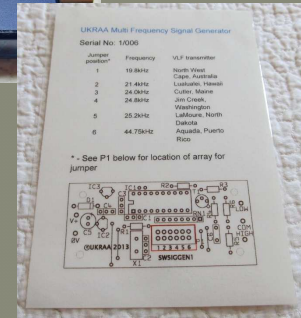
## Optional Components

- Signal generator
  - Single fixed frequency
  - Crystal controlled
- Signal generator
  - Multifrequency
  - Processor controlled



© 2010, 2026 Whitham D. Reeve

17

## Loop Antenna

- Square configuration
- Hardwood frame
- Plywood base
- With proper finishing and without base can be used outdoors



Antenna Tuning Unit →


© 2010, 2026 Whitham D. Reeve

18
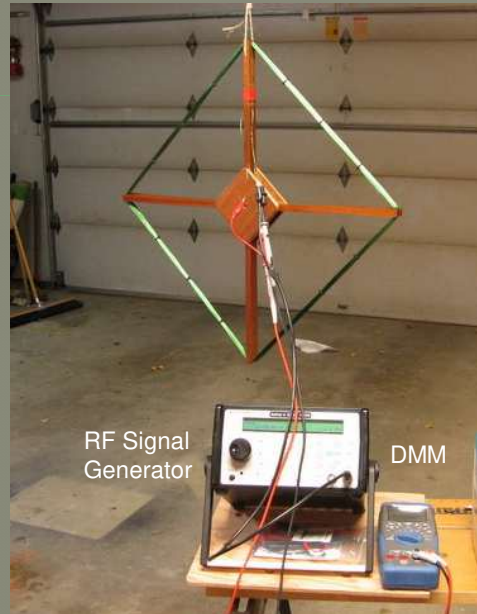
## Loop Characteristics

- Dimensions: 0.4 m sides
- Wire: 24 AWG
- Turns: 125
- Wire length: ~ 203 m
- Inductance: 22.5 mH
- Resistance (dc): 17.1 ohms at 21 °C
- Q: ~ 50 (note)
- Self-resonant frequency: 52.2 kHz (note)

Note: Q and  $F_{sr}$  measured on 137 turn loop



© 2010, 2026 Whitham D. Reeve

19

## Important Loop Parameters

- Inductance (see reference)

$$L = 0.01257 \cdot a \cdot n^2 \cdot \left[ 2.303 \cdot \left( 1 + \frac{b^2}{32 \cdot a^2} + \frac{c^2}{96 \cdot a^2} \right) \log \left( \frac{8 \cdot a}{d} \right) - y_1 + \frac{b^2}{16 \cdot a^2} \cdot y_2 \right]$$

where

- L inductance ( $\mu\text{H}$ )
- a average of inscribed and circumscribed radii (cm)
- b axial dimension of coil cross-section (cm)
- c radial dimension of coil cross-section (cm)
- d diagonal of coil cross-section (cm)
- n number of turns
- $y_1$  value from Table 14, pg 285 of reference based on ratio b/c
- $y_2$  value from Table 14, pg 285 of reference based on c/b

Reference: Eq. 153, pg 252, Circular C74, Radio Instruments and Measurements, US Department of Commerce, National Bureau of Standards, 1937

© 2010, 2026 Whitham D. Reeve

20

## Important Loop Parameters

- Open circuit rms voltage


$$V = 2 \cdot \pi \cdot n \cdot A_e \cdot f \cdot B \cdot \cos(\theta)$$

where

- V open circuit rms voltage (V)
- n number of turns
- $A_e$  Area of equivalent circular loop of radius a (m<sup>2</sup>)
- f frequency (Hz)
- B rms magnetic induction (T)
- $\theta$  angle between magnetic field lines and normal of loop frame (radians)
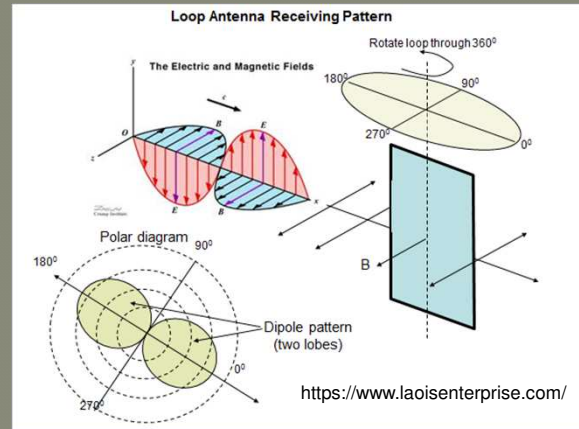
### To increase terminal voltage:

- Increase antenna area,  $A_e$
- Increase number of turns, n
- Increase frequency, f
- Increase magnetic induction, B



## Important Loop Parameters

- Effective Height

$$h_e = \frac{V}{E}$$

where

- $h_e$  effective height (m)
- E rms electric field strength (V/m)
- V open circuit rms voltage (V)

Effective height is a measure of how well the field strength is converted to antenna terminal voltage

- Magnetic induction

$$B = \frac{E}{c}$$


where

- c speed of light ( $3 \times 10^8$  m/s)

## Antenna Q

- Quality Factor (Q)
  - If an external capacitor is connected in parallel with the loop antenna and adjusted to resonate the antenna, the voltage across the terminals increases by the factor Q:

$$V = h_e \cdot E \cdot Q$$

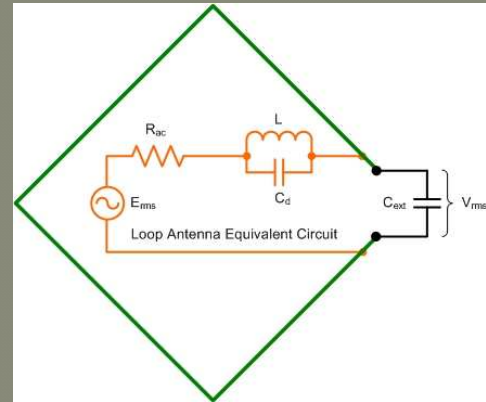

Loop antenna equivalent circuit

## Antenna Q

$$Q = \frac{f_r}{\Delta f}$$

$$Q = \frac{2 \cdot \pi \cdot f_r \cdot L}{R_{ac}}$$


Q measurement made with  
1 Mohm loading was 50

where

$f_r$  resonant frequency (Hz)  
 $\Delta f$  3 dB (power) bandwidth (Hz)  
 $R_{ac}$  equivalent ac resistance of loop winding (ohm)
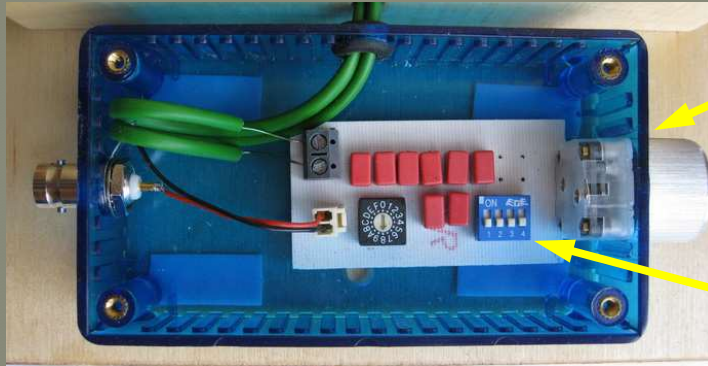
## Antenna Tuning Unit

- ATU improves antenna voltage capture (**resonating capacitor**)
- Also compensates for interconnecting cable capacitance



Variable Capacitor for fine tuning


Fixed capacitors for coarse tuning

© 2010, 2026 Whitham D. Reeve

25

## Antenna Tuning Unit

- Configuration

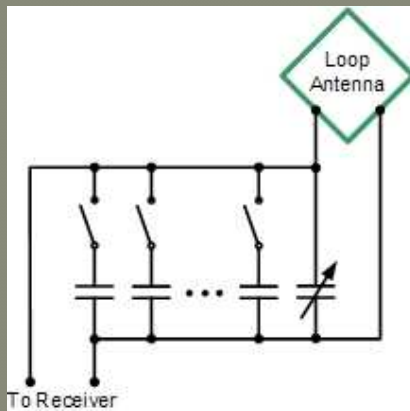

ATU enclosure is not weather resistant

© 2010, 2026 Whitham D. Reeve

26


# Tuning
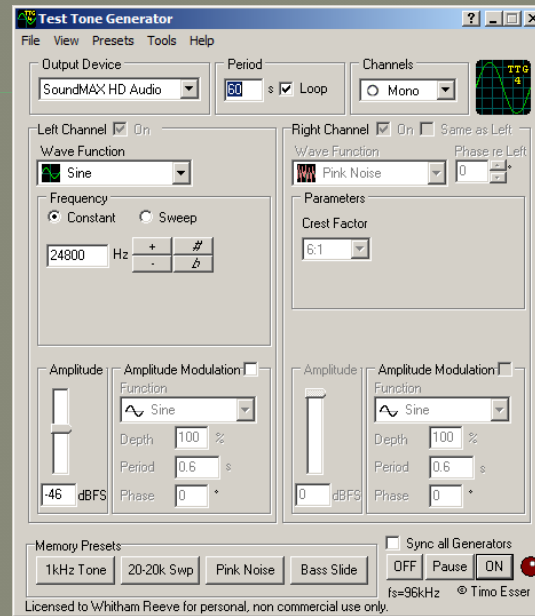
## Signal Generator

- Hardware based



- Hardware and software based
  - PC soundcard
  - Test tone generator software




© 2010, 2026 Whitham D. Reeve

27
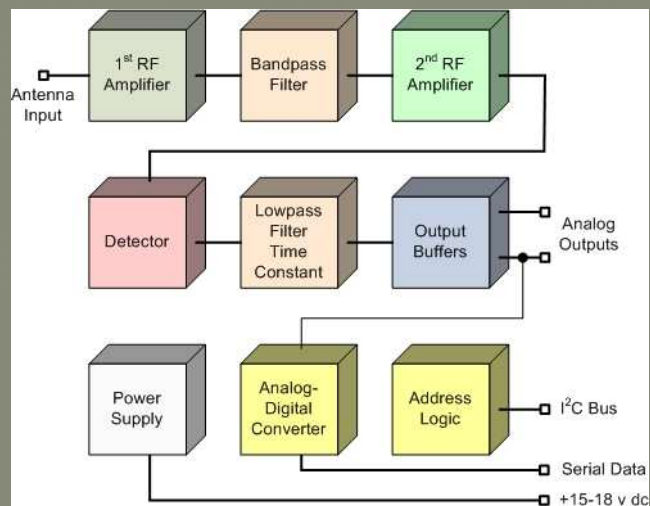
# VLF Receiver Module

- Receiver is a tunable audio frequency amplifier with an envelope detector



© 2010, 2026 Whitham D. Reeve

28

## Receiver Specifications

Parameter	Value
Frequency range	10 to 35 kHz
RF input impedance	~ 1 Mohm unbalanced
Minimum discernible signal voltage	~ 30 $\mu$ V
Analog output voltage	No. 1: 0 to 5 V dc No. 2: 0 to 2.5 V dc
Optional input	Auxiliary input to channel 1 of onboard ADC
Power	15 to 18 V dc, ~ 35 mA


© 2010, 2026 Whitham D. Reeve

29

## Receiver Stages

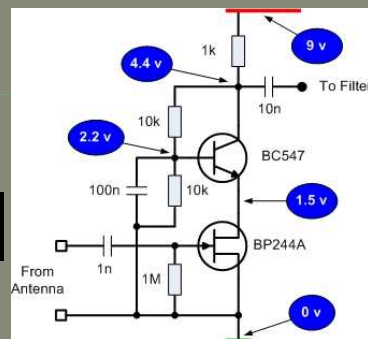
### 1<sup>st</sup> RF Amplifier

Cascode configuration, ~ 1.5X Voltage Gain  
Externally tuned


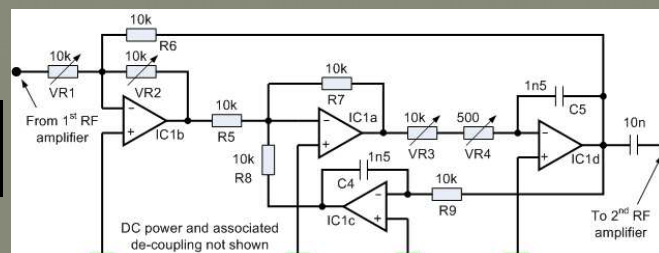
### Bandpass filter

Almost independent tuning, gain and Q  
Bi-Quadratic Filter (State Variable Filter)  
1X Voltage Gain




© 2010, 2026 Whitham D. Reeve

30

# Receiver Stages

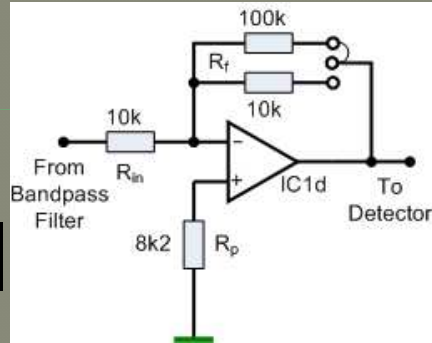
## 2<sup>nd</sup> RF Amplifier

Inverting amplifier X1 or X10 Voltage Gain  
Untuned


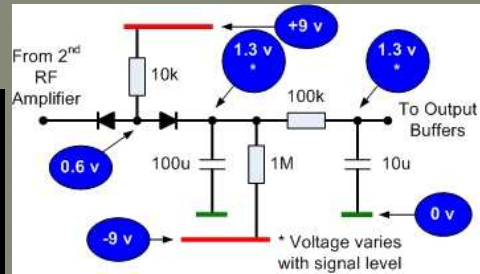
## Detector & Lowpass Filter

Time constants:  
1 second (100 kohm : 10 uF)  
100 seconds (1 Mohm : 100 uF)  
~ 1 second rise time  
~ 40 second fall time




© 2010, 2026 Whitham D. Reeve

# Receiver Stages
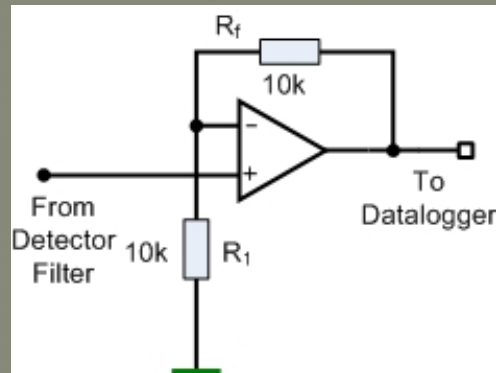
## Output Buffers

Dual Non-Inverting Amplifiers  
1X (0 to 2.5 V output) Voltage Gain  
2X (0 to 5.0 V output) Voltage Gain



© 2010, 2026 Whitham D. Reeve


## Receiver Options

### Printed Circuit Board On-Board Options

- Provisions for a MAX186 analog-digital converter (ADC) IC
  - Compatible with PC parallel printer port and Radio-SkyPipe software

Modern PCs do not have a built-in Parallel Print Port (LPT)

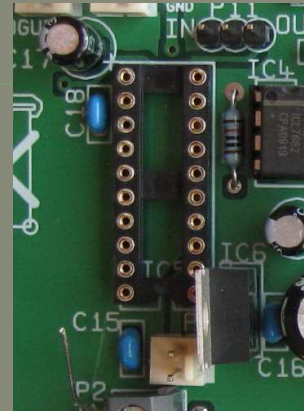- Auxiliary input port for unused channel on ADC
- Option jumpers for selecting the PCB input/output connectors





© 2010, 2026 Whitham D. Reeve

33

## Receiver Options
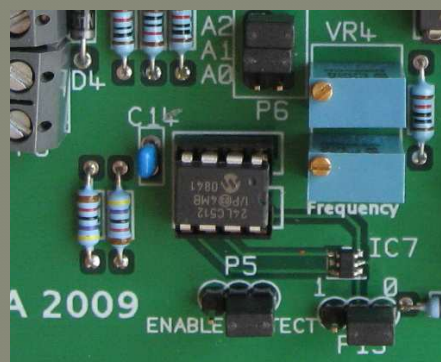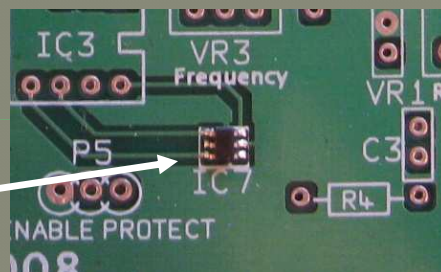
### On-Board Options – Cont'd

- Temperature sensor
  - Uses I<sup>2</sup>C bus for connection to Starbase controller
- Electrically erasable programmable read-only memory (EEPROM) IC
  - Uses I<sup>2</sup>C bus for connection to Starbase controller
  - Sets receiver address
  - Stores configuration attributes



© 2010, 2026 Whitham D. Reeve

34

# KIT CONSTRUCTION



© 2010, 2026 Whitham D. Reeve

35

## Construction

- Antenna



© 2010, 2026 Whitham D. Reeve

36

## Construction

- Receiver Kit
  - Individually bagged and marked parts



© 2010, 2026 Whitham D. Reeve

37

## Construction

- Receiver Assembly
  - Simple enough that few problems will be encountered except
    - Poor soldering
    - Incorrect component placement



Date Stamp 2008 →

© 2010, 2026 Whitham D. Reeve

38

# Construction

- Receiver
  - Completed board is not crowded and solder landings are properly sized for a fine-tip soldering iron

Date Stamp 2009 →



© 2010, 2026 Whitham D. Reeve

# Construction

- Receiver No. 1

For reference, analog meter is ~ 40 mm square



© 2010, 2026 Whitham D. Reeve

## Construction

- Receiver No. 2

For reference,  
analog meter is  
~ 40 mm square



## Construction

- Receivers



# PERFORMANCE



© 2010, 2026 Whitham D. Reeve

43

## Performance ~ Live


- Considerable difficulty encountered with reliably receiving VLF transmissions in Anchorage, Alaska
  - Persistent local interference
  - Distance from transmitter stations
  - Northern latitude propagation
- Testing performed indoors during the winter
  - No opportunity to move antenna outdoors and away from potential interference sources



© 2010, 2026 Whitham D. Reeve

44

# Performance ~ Live

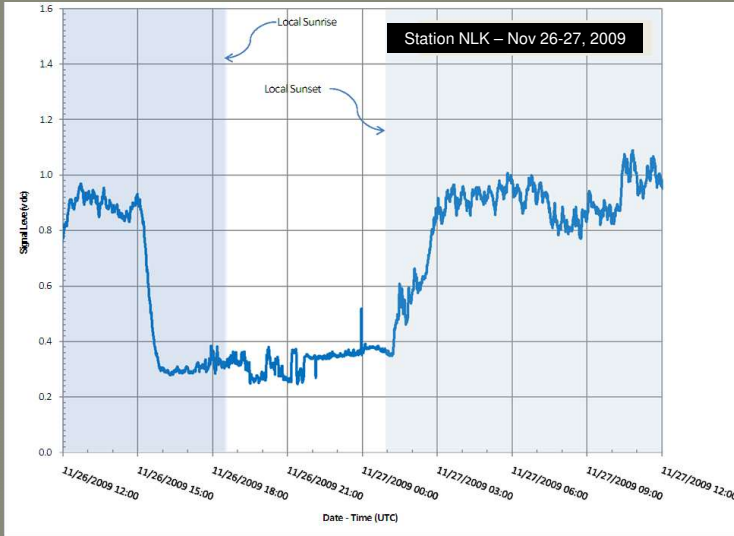


Jim Creek, Washington  
24.0 kHz: Day 1

### Characteristic Trace:

- ✓ Noisy at night but higher signal level
- ✓ Signal level dip at sunrise and sunset
- ✓ Lower but relatively steady signal level during daytime
- ✓ Nighttime and daytime depend on path

© 2010, 2026 Whitham D. Reeve

# Performance ~ Live

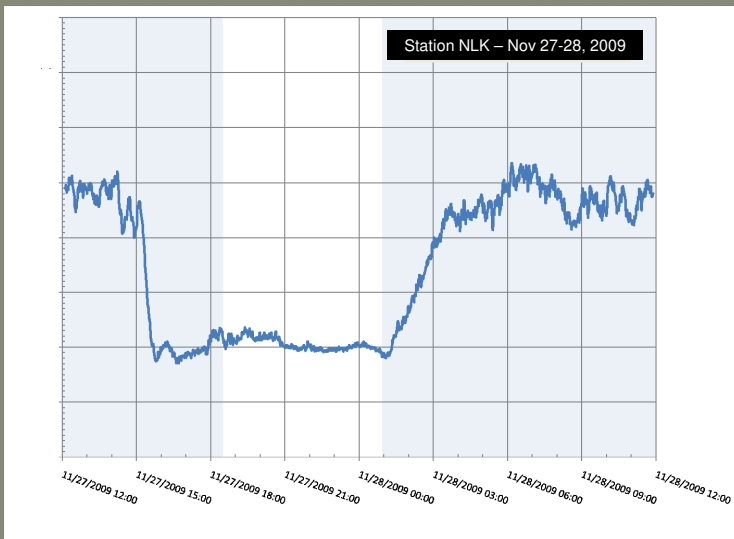

Jim Creek, Washington  
24.0 kHz: Day 2

© 2010, 2026 Whitham D. Reeve


# Performance ~ Live



Jim Creek, Washington  
24.0 kHz: Day 3

© 2010, 2026 Whitham D. Reeve
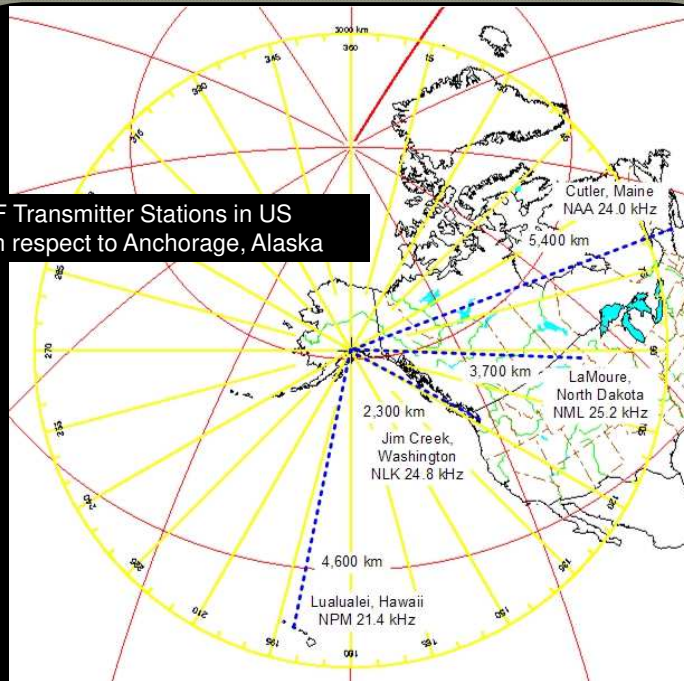
## VLF Transmitter Stations in US with respect to Anchorage, Alaska



© 2010, 2026 Whitham D. Reeve

## Improving Performance

- Where the distance between the transmitter and receiver exceeds around 1,000 km, a larger antenna may be advisable
- Existing square loop design can be scaled up to any practical dimension
- Attention will need to be paid to the self-resonant frequency due to distributed capacitance of the windings
  - Self-resonant frequency > operating frequency

## Improving Performance

- Slight redesign of the 1st RF input amplifier to increase its gain
- Add a preamplifier with balanced low impedance input and unbalanced high impedance output to better match antenna to 1<sup>st</sup> RF amplifier
- Replace inexpensive TL084 IC used for bandpass filter with a higher performance quad op-amp
- Tweak bandpass filter circuit to reduce the chance of oscillation at high Q settings
- Shield stages to reduce undesired feedback

# CONCLUSIONS




© 2010, 2026 Whitham D. Reeve

51
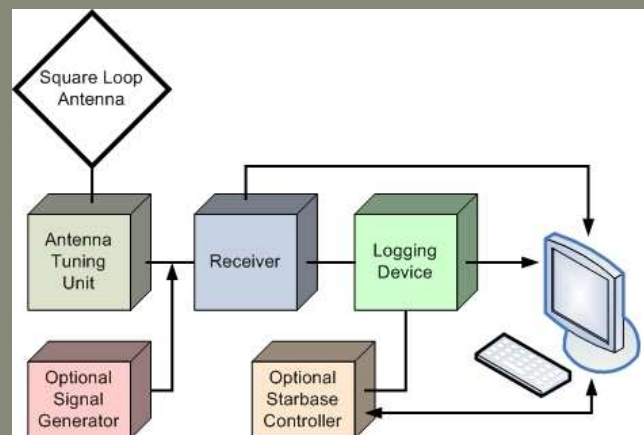
## Conclusions

- The UKRAA VLF Receiver System consists of
  - Loop antenna
  - Antenna tuning unit
  - **Tunable** Receiver
  - **Accessories**
- Available in kit form or already built



© 2010, 2026 Whitham D. Reeve

52

## Conclusions

- Receiver design is unique among units used by amateur radio astronomers
  - Used with considerable success in the UK and Europe
  - Antenna and receiver input circuits are designed for receiving conditions in that region, where suitable VLF transmitters are less than 1,000 km away

## Conclusions

- Receiver should work well in much of the US
  - Considerable difficulty has been encountered in **Anchorage**, Alaska reliably receiving stations because of local interference and distance to stations
  - Larger antenna may be necessary in some locations

# END OF PRESENTATION

!

CONTACT:  
[whitreeve@gmail.com](mailto:whitreeve@gmail.com)



© 2010, 2026 Whitham D. Reeve